

VIVEKANAND COLLEGE, KOLHAPUR
(An Empowered Autonomous Institute)

B.Sc. Part-I (Electronics) (Sem-II)

Internal Examination March-2025

Course name & Course Code: Digital Electronics-II: 2DSC03ELE22

Date: 11/03/2025

Time: 30 min

Marks: 10

Q.1) Select the correct alternative (one mark each)

(02)

1. Positive edge-triggered flip-flop changes its state on _____.
 - a. Low-to-high transition of clock
 - b. High-to-low transition of clock
 - c. Enable input (EN) is set
 - d. Preset input (PRE) is set
2. The Preset and Clear are _____-inputs in the flip-flops.
 - a. Synchronous
 - b. Asynchronous
 - c. Control
 - d. None of the Mentioned

Q.2) Attempt any TWO (4 marks each)

(08)

1. Explain working of RS Latch using NOR gates
2. Explain working of D flip-flop with suitable diagram
3. Describe the working of JK flip flop with circuit diagram and truth table
4. What is the role of preset and clear terminal of flip-flop with suitable example?

Shri Swami Vivekanand Shikshan Sanstha's
VIVEKANAND COLLEGE, KOLHAPUR (An EMPOWERED AUTONOMOUS INSTITUTE)
B.Sc. I Sem II Internal Exam March 2025
Paper: Digital Electronics-II Code: 2DSC03ELE22

Date: 11/03/2025

Sr. No.	Roll No	StudentName	Sign
1	7210	SAYYAD ARFA PARVEJ	AB
2	7211	SHAIKH ALISHA YASIN	Alshoikh.
3	7229	ADISARE GANESH DILIP	AB
4	7230	DIXIT SAMRUDDHI SATYA	Dixit
5	7231	MULLA SAJID FIROJ	Mulla
6	7232	PARALE ABHISHEK SAMBHAJI	8
7	7233	PATIL PRATIKSHA PRAKASH	AB
8	7234	RAM ARCHANAKUMARI DAROGA	AB
9	7235	GHATGE RANJIT SACHIN	Ran
10	7236	KOLI SAMARTH BALASAHEB	S.B. Koli
11	7237	KUMBHAR ADITI SANDIP	Aditi Kumbhar
12	7238	METHE NIKHIL KRISHNAT	NKmethe
13	7239	PATIL AMIT SADASHIV	AB
14	7240	PATIL OMKAR BHAUSO	AB
15	7241	POWAR SAMRUDDHI KRUSHNAT	Powar
16	7242	RUPNAR PANDURANG MARUTI	AB
17	7243	THAKARE PARAS PRAKASH	AB
18	7244	GAIKWAD PRANALI RAMESH	Pranali
19	7245	PATIL ANUSHKA JINGONDA	Anushka
20	7246	PATIL ATHARVA RAJARAM	APPatil
21	7247	SUTAR SHRUTI ANANDA	S. A. Sutar
22	7267	CHANDREKAR VIGHNESH RAJESH	Chandekar
23	7268	INDULKAR KSHITIJA ATUL	Indulkar
24	7269	KUMBHAR JAYDEEP SHANKAR	KB
25	7270	KUWALEKAR Koustubh Bhaskar	Koustubh
26	7271	LOKHANDE APURVA DILIP	Lokhande
27	7272	MALAGE PRATIKRAJ JAYKUMAR	Pratik
28	7273	MANE AVIRAJ BALKRISHNA	A.B. Mane.

Sr. No.	Roll No	StudentName	Sign
29	7274	MASARANKAR SAMIKSHA GOVIND	
30	7275	MOHITE ARJUN KIRAN	
31	7276	PATIL ADITYA SHIVAJI	
32	7277	PATIL RAJWARDHAN SHRIRAM	
33	7278	PATIL SANKET SANDIP	
34	7279	RAUT SIDDHI SHIVAJI	
35	7280	THORAWADE SHIVRAJ RAMCHANDRA	
36	7281	BHOJE SHRADHA SACHIN	
37	7282	BOGARE SARTHAK VISHWANATH	
38	7283	CHOUGALE AYUSH BALAVANT	
39	7284	GARDI SAYMA RASHID	
40	7285	HAVALDAR HARSHA BALASO	
41	7286	KAMAT SHRIVEN SANDIP	
42	7287	KIRAMATE SAKSHI SURESH	
43	7288	KOLI SAMIKSHA SANTOSH	
44	7289	KUMBHAR GOURI TANAJI	
45	7290	KUMBHAR SIDDHI UDAY	
46	7291	KUPALE AKSHAY SHIVAJI	
47	7292	PATIL AISHWARYA BABASO	
48	7293	RATHOD LAXMI MACHHINDRA	
49	7294	SATARMEKAR NIDA NISARAHAMAD	
50	7295	SHINDE ANNADA SURAJ	
51	7328	JOHAR ADARSH RAVINDRA	
52	7529	SHINDE SHREEYASH FIRO	
53	7530	KADAM PAVAN BAJIRAO	
54	7539	BELEKAR SHUBHAM ANI	
55	7550	Dinesh Dattatray Mame	
	7548	AYYAN, PARVEZ, PATIL	

7888000



(अधिकारप्रदत्त स्वायत्त)
कोल्हापूर

VIVEKANAND COLLEGE, KOLHAPUR.
(Empowered Autonomous)

SUPPLIMENT

08/10/2022
॥ ज्ञान, विज्ञान आणि सुसंस्कार यासाठी शिक्षण प्रसार ॥
Name - Same
BSC - I (Sem II)
Subject - Digital Elec.
- शिक्षणमहर्षी डॉ. बापूजी साबुंबे
Course code - 2DSC03ELE22

Jr. Supervisor's Sign. :

Students Sign. : S. Dixit

Seat No. : 7230

Seat No. in words :

Suppliment No. :

15753

Centre

प्र. क्र.
Q. No.

Q1)

1) Positive edge-triggered flip-flop change its state on
→ a) Low-to-high transition of clock.

2) The Preset and Clear are inputs in the flip-flop
→ c) Control.

(अधिकारप्रदत्त स्वायत्त)

कोल्हापूर


प्र. क्र.
Q. No.

Q2)

3)

 $\Rightarrow$

clocked JK flip flop [level clocked]

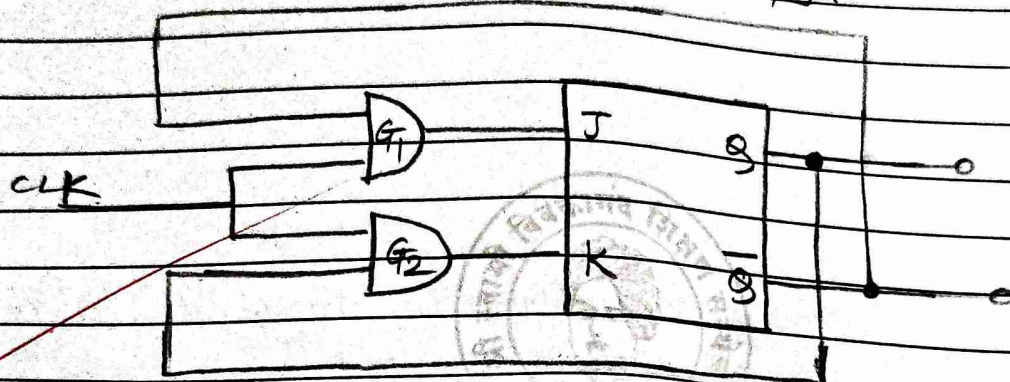

A J-K Flip flop consists of two AND gates with inverted output signals compared to R-S Flip-flop. The output conditions of AND gate is that if any of inputs is low then the output is also low.

Truth Table :	CLK	J	K	Action/Output
	X	X	X	$Q_n (L \cdot S)$
	0	X	X	$Q_n (L \cdot S)$
	1	0	0	$Q_n (L \cdot S)$
	1	0	1	0 (Reset)
	1	1	0	1 (set)
	1	1	1	$\overline{Q_n} (L \cdot S) /$ Toggle

Working :

Case I : CLK = 0 (Low)

When $CLK = 0$, both J & K input signals enter do-not care condition, and their output signal reaches Last State

State
Here $Q_{n+1} \Rightarrow$ Output signal ~~before~~ after clock is low.

$Q_{n+1} \Rightarrow$ Output signal before clock is low.

Case II : CLK = 1 (High)

Case II : $CLK = 1$ (High)

When clock is high the further following cases of input and output are obtained, which are given as-

g) $J = 0, K = 0$ (CLK = 1)

With both the inputs low ($J=K=0$) the two AND gates G_1 and G_2 remain disabled according to the condition of AND.

$$\therefore Q = \overline{Q} = Q_n$$

$\therefore Q = \overline{Q} = Q_n$
Hence the output remains in last state

b) $J = 0, K = 1$ (CLK = 1)

With inputs $J=0, K=1$, the AND gate G_2 only get activated and G_1 remains disabled

$$\therefore Q = 0, \quad \bar{Q} = 1$$

$\therefore Q = 0, \bar{Q} = 1$
This condition is called RESET condition.

c) $J=1, K=0$ (CLK=1)

With $J=1$, $K=0$ ($CLK=1$)
 With $J=1$, Q_1 gates get active and gives $Q=1$ and
 as $K=0$ we get $\bar{Q}=0$
 SET condition

as $K=0$ we get
This condition is called SET condition.

d) $J=1, K=1$

$J=1, K=1$
Both inputs J & K high, hence, both the AND gates G_1 and G_2 activate simultaneously. This condition is called Toggle and therefore is NOT ALLOWED.



(अधिकारप्रदत्त स्वायत्त)
कोल्हापूर

VIVEKANAND COLLEGE, KOLHAPUR.
(Empowered Autonomous)

SUPPLIMENT

॥ ज्ञान, विज्ञान आणि सुसस्कार यासाठी शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साळुंखे

Course:- 2DSC08ELE22
Digital Electronics
- II

Jr. Supervisor's Sign. :

Students Sign. :

Seat No. : 7267

Seat No. in words : seven thousand two hundred
& sixty seven

Suppliment No. :

15779

Centre Vck

प्र. क्र.

Q. No.

Q. 1

1. Positive edge-triggered flip-flop changes its state on

→ b) High-to-low transition of clock

2. The present & Clear are inputs in the flip-flop.

→ b) Asynchronous

02

Section

Q. No.


Marks

प्र. क्र.

Q. No.

Q. 2.

R-S Latch using NOR gates

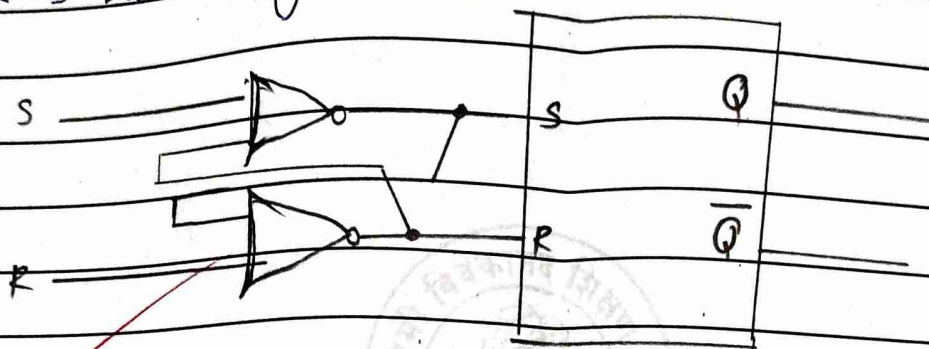Construction:-

- In R-S Latch two NOR gates are used
- When the input In R-S Latch when one of input is high the output becomes low.

Working:-Case I:-When $R=0$ & $S=0$ When R & $S=0$ they go on disabled & contain ^{or go in} forbidden stateCase II:-When $R=0$ & $S=1$ When $R=0$ & $S=1$ then it is in set state

If now one output is high/1 the output is so it is in


set stateWhen Case III:-When $R=1$ & $S=0$

- When $R=1$ & $S=0$ then the output is is 'Reset state'

Case IV :-

When $R=\phi$ & $S=\phi$

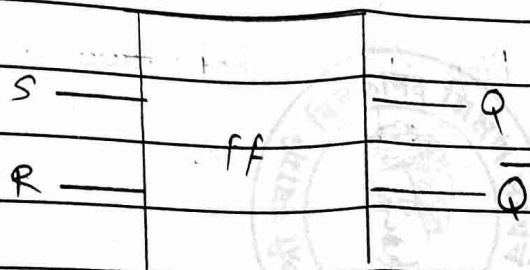
- When $R=1$ & $S=1$ then it is in L.S state it means Last state. It is complementary.



Logic of symbol

Input		Output	Action
R	S		
0	0	for bidden	cross around.
0	1	1	Set
1	0	0	Reset
1	1	L.S	No change

2) D-Flip flop

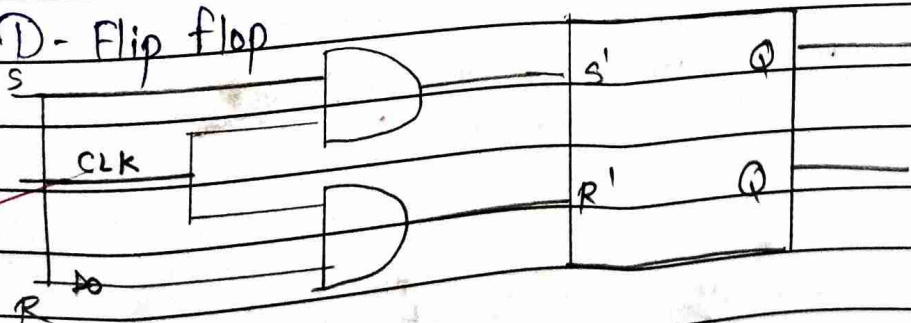

04

Section

Q. No.

Marks

प्र. क्र.
Q. No.

S

R

 $\bar{Q}$ $\bar{Q}$

Logic of symbol.

~~Working:-~~Construction:-

- In D flip-flop it consist two AND & one NOR gate & also using clock
one input is 1

Working:-Case I:-When $D=0$ CLK=0

- When CLK=0 it is not allowed it is complementary 'Clears Data'
- So it is in last state.

Case II:-

When CLK=1

It is an also last state
so these are two state

1) $D=0$:-When it is an $D=0$ then it is an Set state2) $D=1$:-When $D=1$ then it is an Reset state



(अधिकारप्रदत्त स्वायत्त)
कोल्हापूर

॥ ज्ञान, विज्ञान आणि सुसंस्कार यासाठी शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साळुंखे

Jr. Supervisor's Sign. :

Students Sign. :

Seat No. :

Seat No. in words :

Suppliment No. :


15801

Centre

SUPPLIMENT

क्र. No.	Input		Output
	CLK	D	(Q _{n+1})
	0	x	L.S (Q _n)
	1	x	L.S (Q _n)
	1	0	Set
	1	1	Reset

3) Jk flip flop.

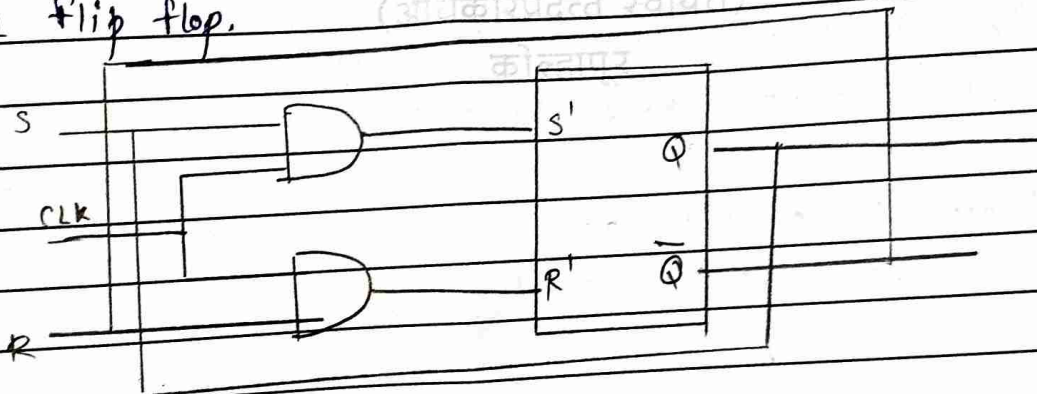

02

Section

Q. No.

Marks

प्र. क्र.
Q. No.

Working :-

Case I :-When $CLK = 0$

- When CLK is 0 is complementary state it is not allowed so it is Last state

Case II :-When $CLK = 1$

- When CLK is 1 it is not allowed it is also Last state
- When $CLK = 1$ it has 4 Values

a) When $R = 0$ & $S = 0$

When R & $S = 0$ is also not allowed it is in L.S (Last state)

b) When $R = 0$ & $S = 1$

When $R = 0$ & $S = 1$ it is in Set state

c) When $R = 1$ & $S = 0$

it is in Reset state

Shree Swami Vivekanand Shikshan Sanstha's
VIVEKANAND COLLEGE, KOLHAPUR
(AN EMPOWERED AUTONOMOUS INSTITUTE)

Class: B.Sc.-I, Semester-II,

Course code: 2DSCO3ELE21

Subject: Analog Electronics II

Time: 02:00 pm to 02:30 pm

Date:-10/03/2025 Marks: 10

Q.1. Select the Correct alternative

[2 M]

i. The number of depletion layers in a transistor is

1. Four
2. Three
3. Two
4. One

ii. The region that has the biggest size in a transistor is

1. collector
2. base
3. emitter
4. collector-base-junction

Q.2 .Attempt any Two (Four mark each)

[8 M]

- 1) Explain DC load line and Q-point.
- 2) Explain construction and working of NPN transistor.
- 3) Explain construction and working of PNP transistor.
- 4) Define α and β ? Derive the relation between them.

Shri Swami Vivekanand Shikshan Sanstha's
VIVEKANAND COLLEGE, KOLHAPUR (An EMPOWERED AUTONOMOUS INSTITUTE)
B.Sc. I Sem II Internal Exam March 2025
Paper: Analog Electronics-II Code: 2DSC03ELE21

Date: 10/03/2025

Sr. No.	Roll No	StudentName	Sign
1	7210	SAYYAD ARFA PARVEJ	AB
2	7211	SHAIKH ALISHA YASIN	Shaiikh.
3	7229	ADISARE GANESH DILIP	AD
4	7230	DIXIT SAMRUDDHI SATYA	Dixit
5	7231	MULLA SAJID FIROJ	Mulla
6	7232	PARALE ABHISHEK SAMBHAJI	8.
7	7233	PATIL PRATIKSHA PRAKASH	AR
8	7234	RAM ARCHANAKUMARI DAROGA	AR
9	7235	GHATGE RANJIT SACHIN	Ran
10	7236	KOLI SAMARTH BALASAHEB	S.B. Koli
11	7237	KUMBHAR ADITI SANDIP	Akumbhar.
12	7238	METHE NIKHIL KRISHNAT	Umethe
13	7239	PATIL AMIT SADASHIV	AR
14	7240	PATIL OMKAR BHAUSO	AR
15	7241	POWAR SAMRUDDHI KRUSHNAT	Powar
16	7242	RUPNAR PANDURANG MARUTI	AR
17	7243	THAKARE PARAS PRAKASH	AR
18	7244	GAIKWAD PRANALI RAMESH	Gaikwad
19	7245	PATIL ANUSHKA JINGONDA	Patil
20	7246	PATIL ATHARVA RAJARAM	Patil
21	7247	SUTAR SHRUTI ANANDA	S.A. Sutar.
22	7267	CHANDREKAR VIGHNESH RAJESH	Chand
23	7268	INDULKAR KSHITIJA ATUL	Indulkar
24	7269	KUMBHAR JAYDEEP SHANKAR	K
25	7270	KUWALEKAR Koustubh Bhaskar	Ku
26	7271	LOKHANDE APURVA DILIP	Lokhande
27	7272	MALAGE PRATIKRAJ JAYKUMAR	Malage
28	7273	MANE AVIRAJ BALKRISHNA	A.B. Mane

Sr. No.	Roll No	StudentName	Sign
29	7274	MASARANKAR SAMIKSHA GOVIND	
30	7275	MOHITE ARJUN KIRAN	
31	7276	PATIL ADITYA SHIVAJI	
32	7277	PATIL RAJWARDHAN SHRIRAM	
33	7278	PATIL SANKET SANDIP	
34	7279	RAUT SIDDHI SHIVAJI	
35	7280	THORAWADE SHIVRAJ RAMCHANDRA	
36	7281	BHOJE SHRADHA SACHIN	
37	7282	BOGARE SARTHAK VISHWANATH	
38	7283	CHOUGALE AYUSH BALAVANT	
39	7284	GARDI SAYMA RASHID	
40	7285	HAVALDAR HARSHA BALASO	
41	7286	KAMAT SHRIVEN SANDIP	
42	7287	KIRAMATE SAKSHI SURESH	
43	7288	KOLI SAMIKSHA SANTOSH	
44	7289	KUMBHAR GOURI TANAJI	
45	7290	KUMBHAR SIDDHI UDAY	
46	7291	KUPALE AKSHAY SHIVAJI	
47	7292	PATIL AISHWARYA BABASO	
48	7293	RATHOD LAXMI MACHHINDRA	
49	7294	SATARMEKAR NIDA NISARAHAMAD	
50	7295	SHINDE ANNADA SURAJ	
51	7328	JOHAR ADARSH RAVINDRA	
52	7529	SHINDE SHREEYASH FIRO	
53	7530	KADAM PAVAN BAJIRAO	
54	7539	BELEKAR SHUBHAM ANI	
55	7550	Dinesh Pattatray mane	
56	7241	Samriddhi Kanchit Poo	Signature
	7548	AYYAN P. PATE	
	7548	AYYAN PARVET PATE	



(अधिकारप्रदत्त स्वायत्त)
कोल्हापूर

॥ ज्ञान, विज्ञान आणि सुसंस्कार यासाठी शिक्षण प्रसार ॥

- शिक्षणमहर्षी डॉ. बापूजी साळुंखे

Date & 10/03/2025
Pepper & Analog
Electronics

VIVEKANAND COLLEGE, KOLHAPUR.

(Empowered Autonomous)

Course code & 20SC03ELE21

SUPPLIMENT

10
10

Jr. Supervisor's Sign. :

Students Sign. :

Seat No. : 7237

Seat No. in words :

Suppliment No. :

15934

Centre : Nc 1c

प्र. क्र.

Q. No.

1] 3. Two


2] 2. Collector

(अधिकारप्रदत्त स्वायत्त)
कोल्हापूर

प्र. क्र.
Q. No.

2]

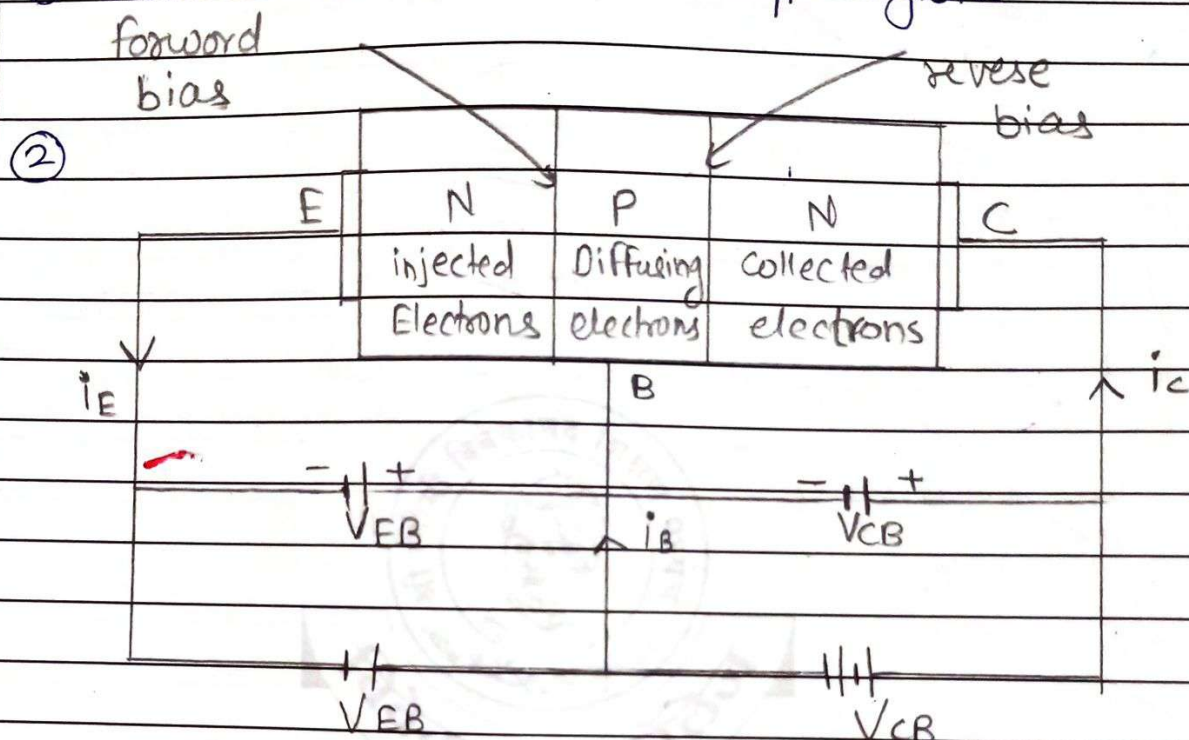Q] ① NPN is a type of transistor where P-region of transistor is sandwiched between two N-type regions.



② As shown in the figure forward bias to ~~emitter~~ emitter base junction start flow of electrons towards P region. that causes to constitute current I_E . In P region Base is lightly doped because of that in P region just 2% of all flow of electrons entering from a become able to collabarat / intersect with holes in P. Remaining 98% electrons flow towards collector region. Diffusing process in P region constitute to I_B current flow. In collector region electrons that remaining in P are collected. because of this process they ~~causes~~ causes to constitute current I_C . The whole current I_E is divided in I_C and I_B . After observing that process we concluded that the Emitter current I_E is the sum of I_C and I_B .

Q. No.

$$I_E = I_C + I_B \quad \text{--- (1)}$$

Q. No.

4] ① α is defined as the current gain of transistor to CB (Common Base configuration).

$$\alpha_{dc} = \frac{I_C}{I_E}$$

② β is defined as the current gain of transistor to CE (Common Emitter configuration)

$$\beta_{dc} = \frac{I_C}{I_B}$$

③ Relation between α and β .

we know the eqⁿ

$$I_E = I_C + I_B \quad \text{--- (1)}$$

let divide eqⁿ (1) by I_C .

$$\frac{I_E}{I_C} = \frac{I_C}{I_C} + \frac{I_B}{I_C}$$

$$\alpha_{dc} = 1 + \frac{1}{\beta_{dc}}$$

$$\frac{1}{\alpha_{dc}} = \frac{\beta_{dc} + 1}{\beta_{dc}}$$

$$\boxed{\alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}}} \quad \text{--- (2)}$$

similarly,

$$\frac{1}{\beta_{dc}} = \frac{1}{\alpha_{dc}} - 1$$

04

Section

Q. No.

Marks

प्र. क्र.
Q. No.

$$\frac{1}{\beta_{dc}} = \frac{\alpha_{dc} + 1}{\alpha_{dc}}$$

$$\boxed{\beta_{dc} = \frac{\alpha_{dc}}{(\alpha_{dc} - 1)}} \quad \text{--- (2)}$$

~~The The~~

These both are the relation between α and β .



(अधिकारप्रदत्त स्वायत्त)
कोल्हापूर

VIVEKANAND COLLEGE, KOLHAPUR.
(Empowered Autonomous)

SUPPLIMENT

9/10

Class - BSC (I, Sem II)

Subject - Analog Elec.
- शिक्षणमहर्षी डॉ. बापूजी साळुंखे
Code - 2DSCO3ELE21

Jr. Supervisor's Sign. :

Students Sign. : S. Dixit

Seat No. : 7230

Seat No. in words :

Suppliment No. :

15921

Centre

प्र. क्र.
Q. No.

Q1)

1) The number of depletion layers in a transistor is
→ ~~b) Three~~ c) Two.

2) The region that has the ~~highest~~ biggest size in a transistor
is

0

प्र. क्र.

Q. No.

Q2)

4)

⇒ a) α - The current gain between the common-emitter configuration is α . It is also defined as the ratio of collector current to the emitter current i.e. I_c & I_E respectively.

$$\alpha = \frac{I_c}{I_E}$$

b) β - The current gain between the common-base configuration is called as β . It is also defined as the ratio of collector current to the base current i.e. I_c & I_B respectively. $\Rightarrow \beta = \frac{I_c}{I_B}$

c) Relation between α and β .

As we know that, $I_E = I_c + I_B$ ——— (1)

Emitter current is the sum of collector (cut-off) current and base current.

From the equation of α we get,

$$I_c = \alpha \cdot I_E \text{ ——— (II)}$$

And from the equation of β we get,

$$I_B = \beta \cdot I_E \text{ ——— (III)}$$

∴ Substituting eqⁿ (II) & (III) in eqⁿ (1) we get,


$$I_E = \alpha I_E + \beta I_E$$

$$I_E = (\alpha + \beta) I_E$$

$\therefore \alpha = 1 - \beta$

or $\beta = 1 - \alpha$

Q2)

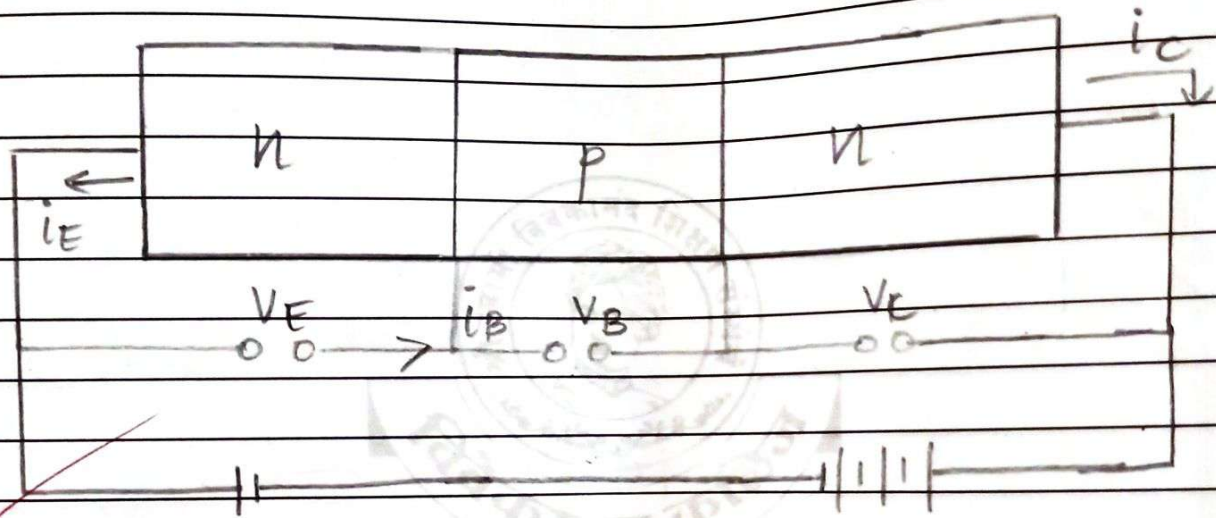

The above figure shows NPN transistor with emitter-base forward biasing and collector base reverse biasing.

The electrons travel from n-region to p-region to combine with holes and gives rise to emitter current I_E in the direction shown in the figure. As the transistor is lightly doped and very thin, only 2% of electrons remain in p-region to combine with holes and the other remaining 98% travel to n-region to form collector current I_C .

This behaviour further tells that the emitter current is the summation of collector current & base current

$\therefore I_E = I_C + I_B$